



The C2 capacitor can be left completely away, in case the coil is driven in an optimal way. This can be done by choosing the right coil inductance and the right parameter set to be trimmed (refer to the MLX10801 IC specification for details).

### 3.3. Optimising the board design


The optimal capacitances found for the tested board are **no absolute values**. They depend very much on the PCB as resonances can arise from the board itself due to parasitics. This is especially true for boards not optimised for good emission behaviour. An EME optimised PCB could minimise such effects and can also help, to reduce the capacitances in their values and costs.

In general the following rules should be applied:

- Traces should be as short as possible
- L3, C2, D3 and the LED should be placed as close together as possible
- Especially the connection from the IC pin DRVOUT to the coil must be kept short.
- Ground areas should be as large as possible. If a 2 layer PCB is used, one layer should be assigned as ground layer and a good connectivity between both layers should be observed
- C4 should be placed very close to the input connector
- C3 and C1 should be placed close to pin 1 (VS) of the chip; C1 directly to pin 1
- Chose the right coil inductance in conjunction with the right parameter set to be trimmed. This could avoid the use of C2 completely.
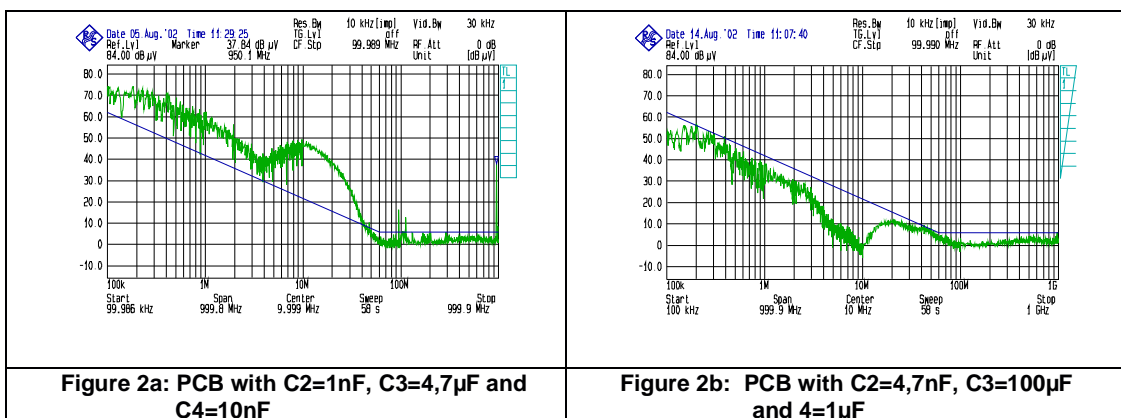
### 3.4. Results

Even without optimising the board layout, great improvements could be achieved by a variation of the capacitances of C2, C3 and C4 as described above. In order to get a better feeling for the results, an *Emission Level Scheme* (according to IEC 61967-4) was implemented into the figures. It shows the maximal allowed emission level for integrated circuits specified by several OEM manufacturers.



## 4. *Immunity to electromagnetic fields*

Tests on component level are currently in progress. Results will be published as soon as they are available. The method used for the test is *Direct Power Injection (DPI)*, a method for conducted coupling of RF power into power and communication lines of the circuit. This method delivers a maximum reproducibility of the measurement results.

For the latest version of this document, go to our website at:

**[www.melexis.com](http://www.melexis.com)**

Or for additional information contact Melexis Direct:

Europe and Japan:	All other locations:
Phone: +32 13 61 16 31	Phone: +1 603 223 2362
E-mail: <a href="mailto:sales_europe@melexis.com">sales_europe@melexis.com</a>	E-mail: <a href="mailto:sales_usa@melexis.com">sales_usa@melexis.com</a>

QS9000, VDA6.1 and ISO14001 Certified