

Table of contents

1	Introduction	2
2	Principle protection circuits	2
2.1	PWM interface 5V level	2
2.2	Protection elements 5V level	3
2.3	PWM interface 12V level	3
2.4	Protection elements 12V level	4
3	General constraints	4
4	Disclaimer	5

1 Introduction

This document describes external protection circuits for 5V digital IOs of MLX81100 in a communication interface to an external ECU in automotive applications. This application note considers two cases:

- 1 PWM interface is running at 5V level
- 2 PWM interface is running at 12V level.

2 Principle protection circuits

All following schematics are sample schematics, which need to be adjusted depending on the application.

2.1 PWM interface 5V level

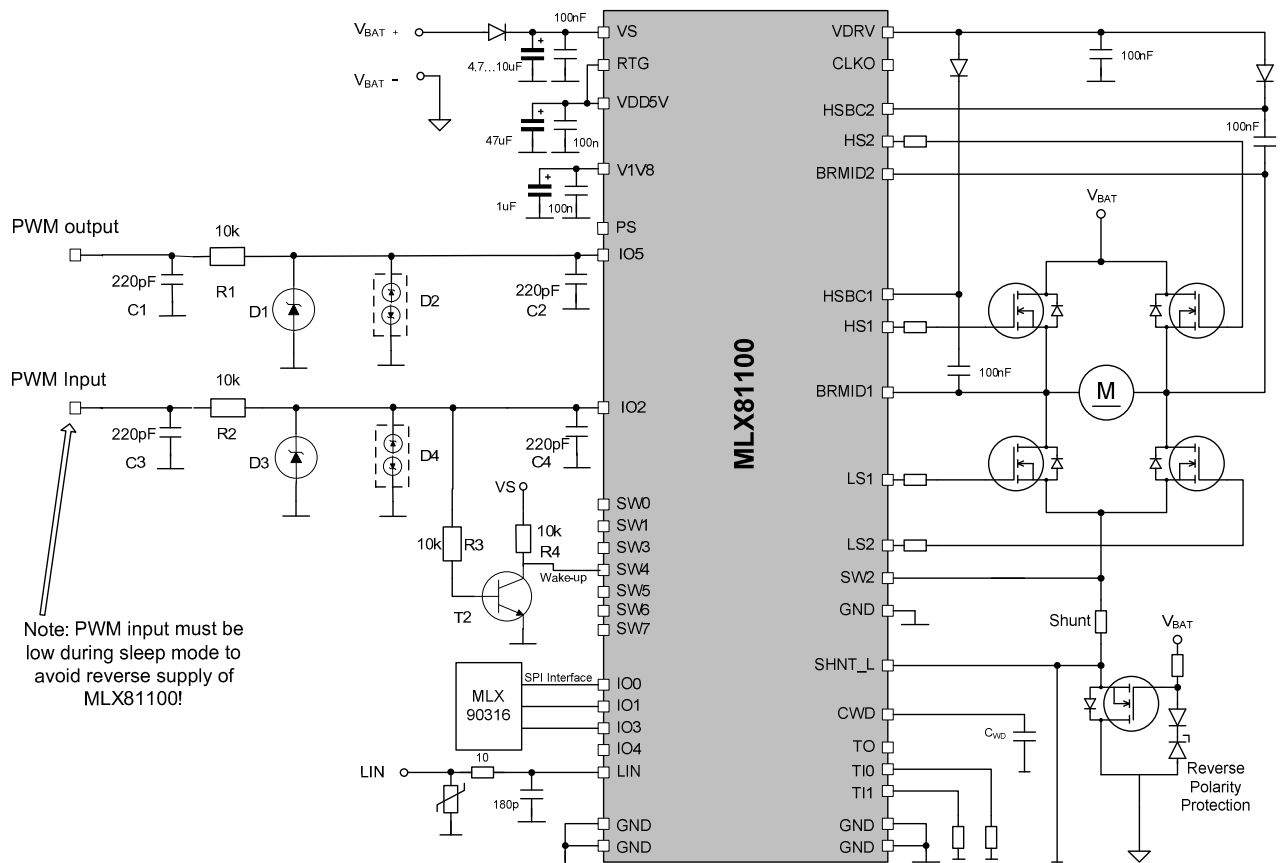


Fig. 1 Sample application circuitry for PWM interface at 5V level


2.2 Protection elements 5V level

Zener diodes D2 and D4: 5,6V zener voltage, different types are available, tests on real chip will help to sort out suitable type, trade-off between fast response according to ESD protection and high power dissipation according to short to Vbat has to be made.

In output path (MLX81100): 5,1V zener diode (D1) with high power dissipation for short circuit protection and fast 5,6V Back-to-back zener diode (D2) for ESD-protection are put in parallel.

Capacitors C1-C4: optional, for improved EMC-behaviour, also tests have to be done.

2.3 PWM interface 12V level

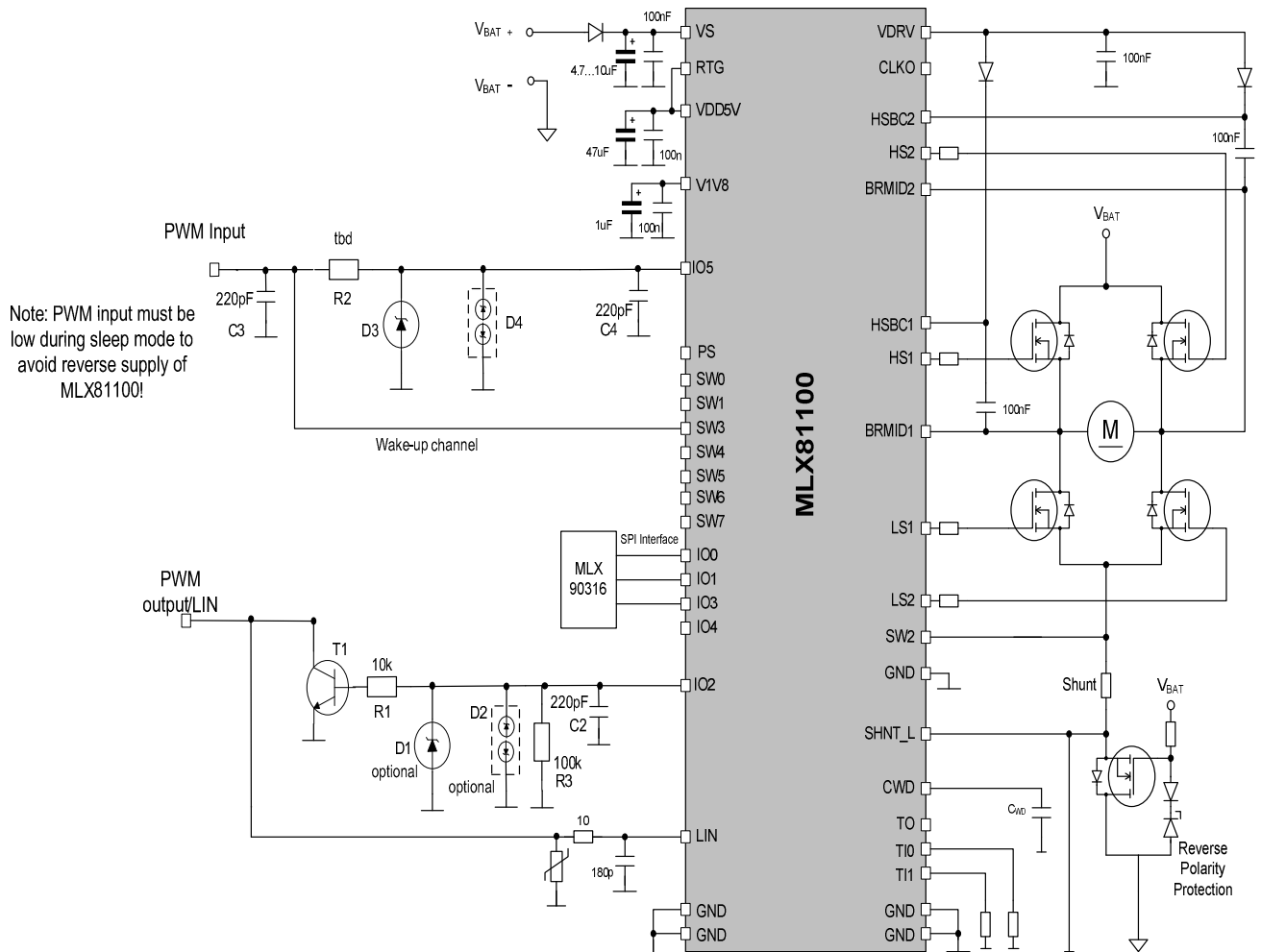

Application circuitry for DC-motor control

Fig. 2 Sample application circuitry for PWM interface at 12V level

2.4 Protection elements 12V level

Zener diodes: 5,6V zener voltage, different types are available, tests on real chip will help to sort out suitable type, trade-off between fast response according to ESD protection and high power dissipation according to short to Vbat has to be made.

Optional:

- In output path (MLX81100): 5,1V zener diode (D1) with high power dissipation for short circuit protection and fast 5,6V Back-to-back zener diode (D2) for ESD-protection in parallel.
- Capacitors C1-C4: for improved EMC-behaviour, also tests have to be done.

3 General constraints

This chapter contains general constraints to be considered when working out an application with PWM interface to an external ECU:

- 1 PWM input of MLX81100 actuator module must be Zero during sleep mode to avoid reverse supply of the chip, which will cause damage or unpredictable behaviour. The soft-/hardware in external ECU has to take care of this.
- 2 In chapter 2.3 the NPN-Transistor T1 inverts the PWM duty cycle, the application software in MLX81100 has to take care of this issue.
- 3 To make the module wake up capable via PWM input a SW pin was connected in both cases in parallel to the PWM input. The general purpose IOs of MelexCM are not wake up capable.
- 4 The general purpose IOs of MelexCM are used because of the need to capture the incoming PWM precisely. At the general purpose IOs of MelexCM a 16-bit timer capture module is present which allows a precise PWM interface. It is not possible to capture the incoming PWM signal with the SW pins directly, there a polling method has to be used.
- 5 To generate a PWM output signal a general purpose IO of MelexCM is connected to the output of PWM block of MelexCM. Advantages of using a PWM block are: it is easy to use and to configure, it is more precise than doing a PWM signal in software, load for the CPU is minimized.

History record

Rev.	No.	Change	Date
1.0	1	Creation	22/03/07
1.1	2	adapted schematics, GND potential inside RPP	01/02/08

4 Disclaimer

Devices sold by Melexis are covered by the warranty and patent indemnification provisions appearing in its Term of Sale. Melexis makes no warranty, express, statutory, implied, or by description regarding the information set forth herein or regarding the freedom of the described devices from patent infringement. Melexis reserves the right to change specifications and prices at any time and without notice. Therefore, prior to designing this product into a system, it is necessary to check with Melexis for current information. This product is intended for use in normal commercial applications. Applications requiring extended temperature range, unusual environmental requirements, or high reliability applications, such as military, medical life-support or life-sustaining equipment are specifically not recommended without additional processing by Melexis for each application.

The information furnished by Melexis is believed to be correct and accurate. However, Melexis shall not be liable to recipient or any third party for any damages, including but not limited to personal injury, property damage, loss of profits, loss of use, interrupt of business or indirect, special incidental or consequential damages, of any kind, in connection with or arising out of the furnishing, performance or use of the technical data herein. No obligation or liability to recipient or any third party shall arise or flow out of Melexis' rendering of technical or other services.

© 2007 Melexis NV. All rights reserved.

For the latest version of this document, go to our website at:

www.melexis.com

Or for additional information contact Melexis Direct:

Europe and Japan:
Phone: +32 1367 0495
E-mail: sales_europe@melexis.com

All other locations:
Phone: +1 603 223 2362
E-mail: sales_usa@melexis.com

ISO/TS 16949 and ISO14001 Certified